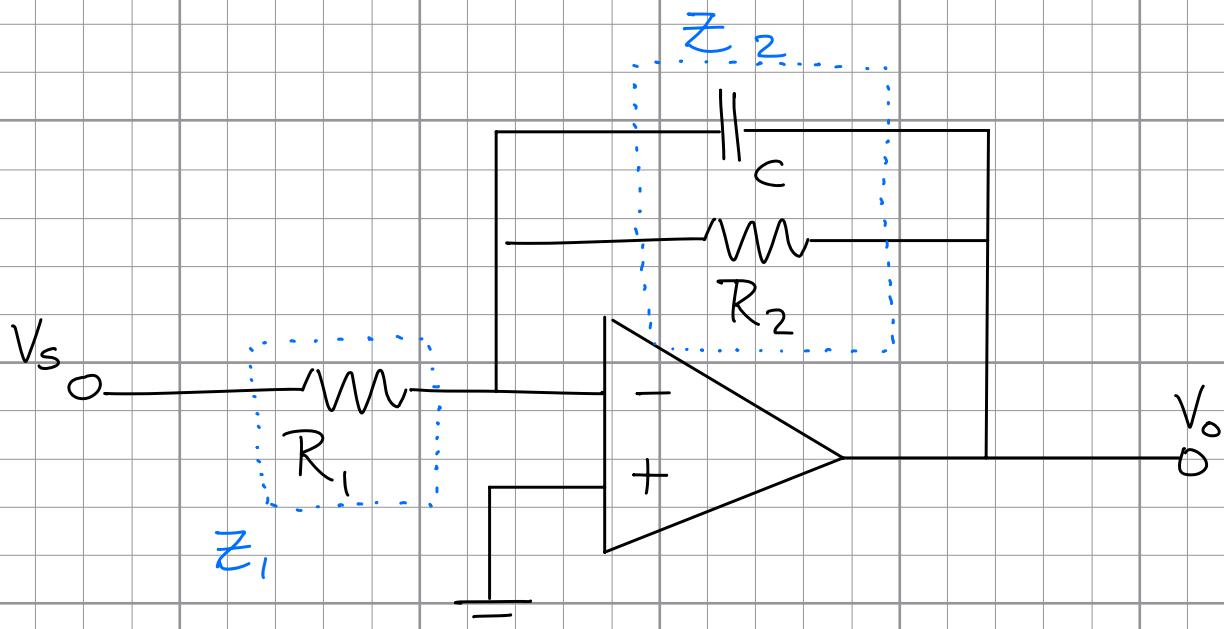


Transfer Function - First-order inverting LPF



Q: What is $H(j\omega)$?

1) Simplify using impedance representation.

$$\begin{aligned} \circ Z_R &= R \\ \circ Z_C &= \frac{1}{j\omega C} = -j(\frac{1}{\omega C}) \end{aligned}$$

2) Use op-amp ideal assumptions
to solve for V_o/V_s .

$$(i) V_- = V_+$$

$$(ii) i_- = i_+ = 0$$

$$1) Z_1 = R_1, \quad Z_{R_2} = R_2, \quad Z_C = \frac{1}{j\omega C}$$

$$\frac{1}{Z_2} = \frac{1}{Z_{R_2}} + \frac{1}{Z_C} \rightarrow Z_{R_2} Z_C = (Z_C + Z_{R_2}) Z_2$$


$$\therefore Z_2 = \frac{Z_{R_2} Z_C}{(Z_C + Z_{R_2})}$$

$$Z_2 = \frac{R_2 \left(\frac{1}{j\omega C} \right)}{R_2 + \frac{1}{j\omega C}} \quad (\text{j}\omega C)$$

$$= \frac{R_2}{j\omega R_2 C + 1}$$

we aim to simplify to:

$$\frac{a+jb}{c+jd}$$

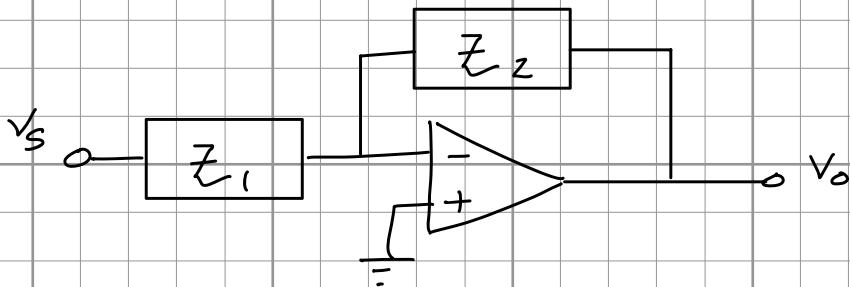

2)


(i) compute voltage at inputs.

(ii) compute current along path.

(i) Note v_+ is held at ground.

$$\therefore v_+ = 0V = v_-$$

(ii) Set-up KCL using other branch.

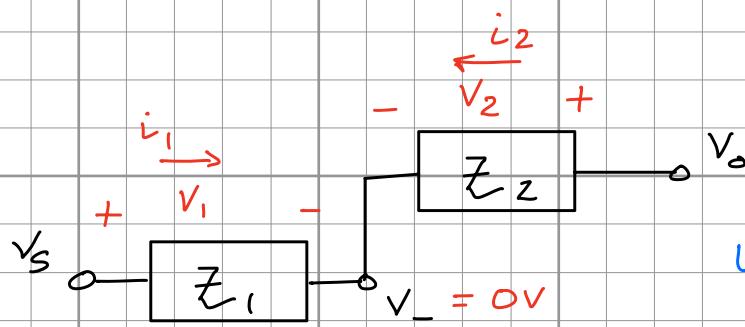

$$\frac{\text{KCL}}{i_1 + i_2 = 0}$$

$$i_1 = -i_2$$

w.r.t. new variables

$$v_o = v_2 = i_2 Z_2$$

$$i_1 = \frac{V_s - V_o}{Z_1} = \frac{V_s}{Z_1}$$

$$i_2 = \frac{V_o - V_-}{Z_2} = \frac{V_o}{Z_2}$$

$$\frac{V_s}{Z_1} = -\frac{V_o}{Z_2}$$

then solve for V_o

$$V_o = -\frac{Z_2}{Z_1} V_s$$

Sub. in expressions for Z_1 & Z_2 .

$$\begin{aligned} \frac{V_o}{V_s} &= -Z_2 \left(\frac{1}{Z_1} \right) \\ &= -\frac{R_2}{1 + j\omega R_2 C} \left(\frac{1}{R_1} \right) \end{aligned}$$

$$\boxed{\frac{V_o}{V_s} = H(j\omega) = -\frac{R_2}{R_1} \left(\frac{1}{1 + j\omega R_2 C} \right)}$$

What is the cutoff frequency?

↪ observe pole location

$$1 + j\omega R_2 C = 0 \rightarrow j\omega = -\frac{1}{R_2 C}$$

compute magnitude & solve for f_c ($\omega = 2\pi f_c$)

$$|j\omega| = \sqrt{\phi^2 + \omega^2} = \omega$$

$$\left| -\frac{1}{R_2 C} \right| = \sqrt{\left(-\frac{1}{R_2 C}\right)^2 + \phi^2} = \frac{1}{R_2 C}$$

$$\omega_c = 2\pi f_c = \frac{1}{R_2 C}$$

$$\therefore f_c = \frac{1}{2\pi R_2 C}$$